


# 09 Logic Blocks

## Arithmetic

©Department of Computer Science  
University of Victoria
 
# Buffer

- A buffer is a gate with the function  $F = X$ :
- As a Boolean function, a buffer is the same as a connection!
- Why use it?
  - A buffer is an electronic amplifier used to improve circuit voltage levels and increase the speed of circuit operation.



## Hi-Impedance Outputs

- Logic gates introduced thus far
  - output values only 0 or 1
  - no outputs connected together
  - transmit signals in *only one* direction
- *Three-state logic* adds a third logic value  
Hi-Impedance (Hi-Z)


thus 3 outputs: 0, 1, and Hi-Z

## Hi-Impedance Outputs (continued)

- What is a Hi-Z value?
  - The Hi-Z value behaves as an open circuit
    - I.e. the output appears to be disconnected
  - It is as if a switch between the internal circuitry and the output has been opened
- Hi-Z may appear on the output of any gate, but we restrict gates to:
  - a 3-state bufferwith one data input and one control input
 
## The 3-State Buffer

- For the symbol and truth table, **IN** is the *data input*, and **EN** the *control input*
- For  $EN = 0$ ,  
→ output = Hi-Z
- For  $EN = 1$ ,  
→ output value = input value
- Variations:
  - IN or EN can be inverted by addition of "bubbles" to signals



Truth Table


EN	IN	OUT
0	X	Hi-Z
1	0	0
1	1	1

# Using tri-state gates to implement an economical multiplexer

When **SelectInput** is high  
→  $F = \text{Input1}$


When **SelectInput** is low  
→  $f = \text{Input0}$

This is really a 2:1 Mux

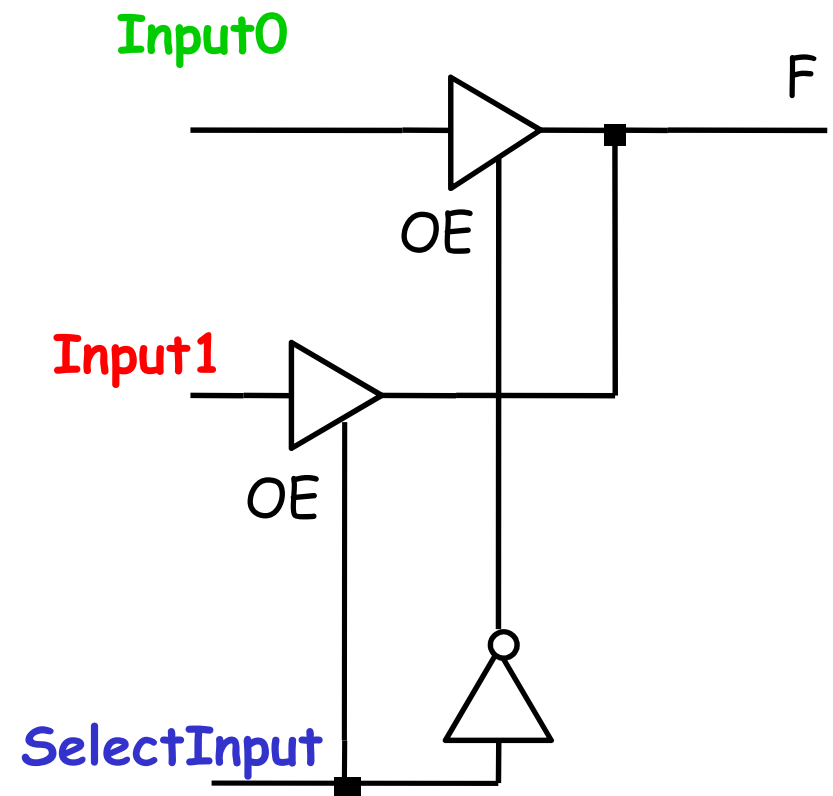
 
# Enabling Function

- *Enabling* permits an input signal to pass through to an output
- *Disabling* blocks an input signal from passing through to an output, replacing it with a fixed value
- The value on the output when it is disabled can be Hi-Z, 0 , or 1



# Arithmetic Overview


- Iterative combinational circuits
- Binary adders
  - Half and full adders
  - Ripple carry and carry lookahead adders
- Binary subtraction
- Binary adder-subtractors
  - Signed binary numbers
  - Signed binary addition and subtraction
  - Overflow
- Binary multiplication
- Other arithmetic functions
  - Design by contraction



# Iterative Combinational Circuits

- Arithmetic functions
  - Operate on binary vectors
  - Use the same subfunction in each bit position
- Can design functional block for subfunction and repeat to obtain functional block for overall function
- *Cell* - subfunction block
- *Iterative array* - a array of interconnected cells
- An iterative array can be in a single dimension (1D) or multiple dimensions

# Block Diagram of a 1D Iterative Array

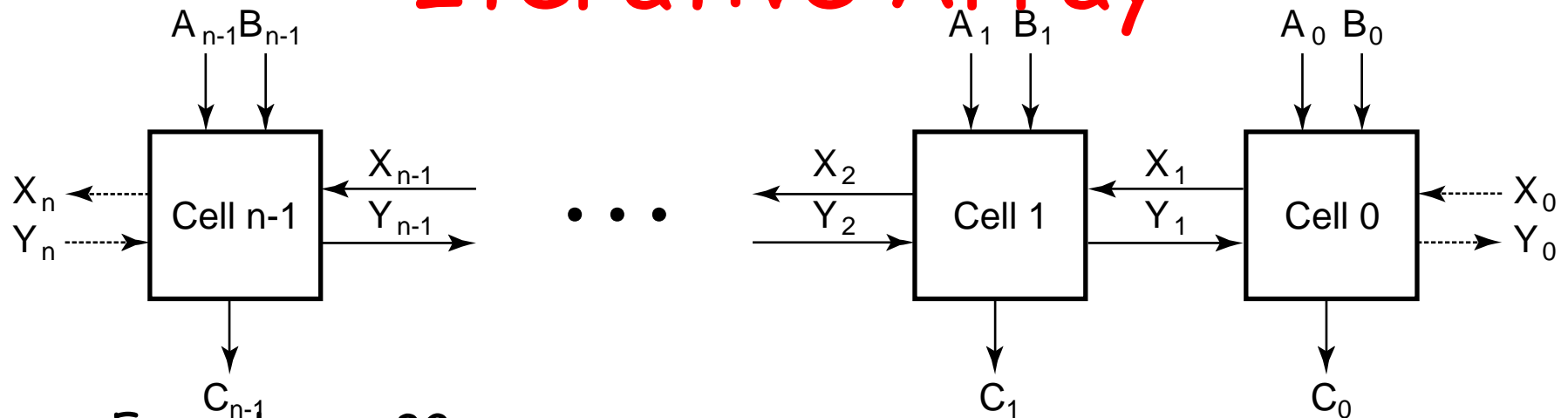

- Example:  $n = 32$ 
  - Number of inputs = ?
  - Truth table rows = ?
  - Equations with up to ? input variables
  - Equations with huge number of terms
  - Design impractical!
- Iterative array takes advantage of the regularity to make design feasible

# Functional Blocks: Addition

- Binary addition used frequently
- Addition Development:
  - *Half-Adder (HA)*, a 2-input bit-wise addition functional block,
  - *Full-Adder (FA)*, a 3-input bit-wise addition functional block,
  - *Ripple Carry Adder*, an iterative array to perform binary addition, and
  - *Carry-Look-Ahead Adder (CLA)*, a hierarchical structure to improve performance.

# Functional Block: Half-Adder

- A 2-input, 1-bit width binary adder that performs the following computations:

X	0	0	1	1
+ Y	+ 0	+ 1	+ 0	+ 1
<hr/>	<hr/>	<hr/>	<hr/>	<hr/>
C S	0 0	0 1	0 1	1 0

- A half adder adds two bits to produce a two-bit sum
- The sum is expressed as a sum bit , S and a carry bit, C
- The half adder can be specified as a truth table for S and C  $\Rightarrow$

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# Logic Simplification: Half-Adder

- The K-Map for  $S, C$  is:
- This is a pretty trivial map!  
By inspection:

$$S = X \cdot \bar{Y} + \bar{X} \cdot Y = X \oplus Y$$

$$C = (X + Y) \cdot \overline{(X \cdot Y)}$$

- and

$$C = X \cdot Y$$

$$C = \overline{\overline{(X \cdot Y)}}$$

- These equations lead to several implementations.

S		Y	
	0	1	1
X	1	2	3

C		Y	
	0	1	
X		2	1

## Five Implementations: Half-Adder

- We can derive following sets of equations for a half-adder:

$$(a) \begin{aligned} S &= X \cdot \bar{Y} + \bar{X} \cdot Y \\ C &= X \cdot Y \end{aligned}$$

$$(d) \begin{aligned} S &= (X + Y) \cdot \bar{C} \\ \bar{C} &= (\bar{X} + \bar{Y}) \end{aligned}$$

$$(b) \begin{aligned} S &= (X + Y) \cdot (\bar{X} + \bar{Y}) \\ C &= X \cdot Y \end{aligned}$$

$$(e) \begin{aligned} S &= X \oplus Y \\ C &= X \cdot Y \end{aligned}$$


$$(c) \begin{aligned} S &= \overline{(C + \bar{X} \cdot \bar{Y})} \\ C &= X \cdot Y \end{aligned}$$

- (a), (b), and (e) are SOP, POS, and XOR implementations for S.
- In (c), the C function is used as a term in the AND-NOR implementation of S, and in (d), the  $\bar{C}$  function is used in a POS term for S.

# Implementations: Half-Adder


- The most common half adder implementation is:  
(e)

$$S = X \oplus Y$$
$$C = X \cdot Y$$

 

- A NAND only implementation is:
 
$$S = (X + Y) \cdot C$$
$$C = ((X \cdot Y))$$



# Functional Block: Full-Adder

- A full adder is similar to a half adder, but includes a carry-in bit from lower stages. Like the half-adder, it computes a sum bit,  $S$  and a carry bit,  $C$ .

- For a carry-in ( $Z$ ) of 0, it is the same as the half-adder:

$Z$	0	0	0	0
$X$	0	0	1	1
$+ Y$	$+ 0$	$+ 1$	$+ 0$	$+ 1$
$C S$	00	0 1	0 1	1 0

- For a carry-in ( $Z$ ) of 1:

$Z$	1	1	1	1
$X$	0	0	1	1
$+ Y$	$+ 0$	$+ 1$	$+ 0$	$+ 1$
$C S$	0 1	1 0	1 0	1 1



# Logic Optimization: Full-Adder

- Full-Adder Truth Table:

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- Full-Adder K-Map:

K-Map for Sum (S):

			Y
	0	1	3
			2
X	1		7
	4	5	6
		Z	

K-Map for Carry (C):

			Y
	0	1	3
			2
X		1	7
	4	5	6
		Z	

# Equations: Full-Adder

- From the K-Map, we get:

$$S = X\bar{Y}\bar{Z} + \bar{X}Y\bar{Z} + \bar{X}\bar{Y}Z + XYZ$$

$$C = XY + XZ + YZ$$

- The S function is the three-bit XOR function (Odd Function):

$$S = X \oplus Y \oplus Z$$

- The Carry bit C is 1 if both X and Y are 1 (the sum is 2), or if the sum is 1 and a carry-in (Z) occurs. Thus C can be re-written as:

$$C = XY + (X \oplus Y)Z$$


- The term  $X \cdot Y$  is *carry generate*.
- The term  $X \oplus Y$  is *carry propagate*.

# Implementation: Full Adder

- Full Adder Schematic
- Here X, Y, and Z, and C (from the previous pages) are A, B,  $C_i$  and  $C_o$ , respectively. Also,  
    G = generate and  
    P = propagate.
- Note: This is really a combination of a 3-bit odd function (for S) and Carry logic (for  $C_o$ ):

(G = Generate) OR (P = Propagate AND  $C_i$  = Carry In)

$$C_o = G + P \cdot C_i$$

 


# Binary Adders

- To add multiple operands, we “bundle” logical signals together into vectors and use functional blocks that operate on the vectors
- Example: 4-bit ripple carry adder: Adds input vectors  $A(3:0)$  and  $B(3:0)$  to get a sum vector  $S(3:0)$
- Note: carry out of cell  $i$  becomes carry in of cell  $i + 1$

Description	Subscript 3 2 1 0	Name
Carry In	0 1 1 0	$C_i$
Augend	1 0 1 1	$A_i$
Addend	0 0 1 1	$B_i$
Sum	1 1 1 0	$S_i$
Carry out	0 0 1 1	$C_{i+1}$

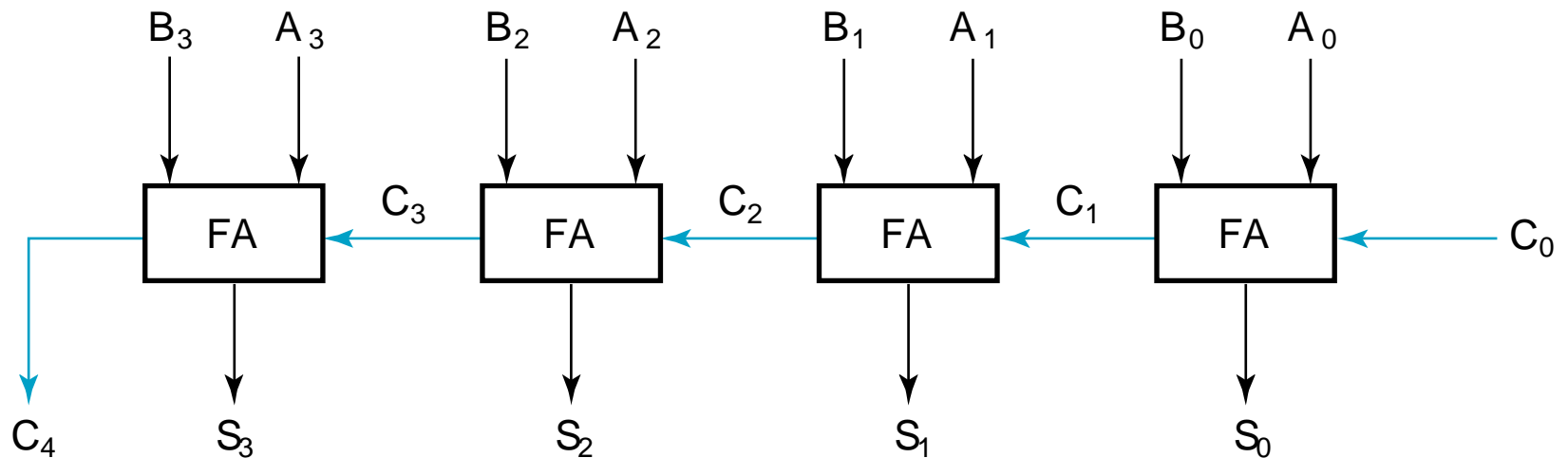
# 4-bit Ripple-Carry Binary Adder

- A four-bit Ripple Carry Adder made from four 1-bit Full Adders:


 
# Carry Propagation & Delay

- One problem with the addition of binary numbers is the length of time to propagate the ripple carry from the least significant bit to the most significant bit.
- The gate-level propagation path for a 4-bit ripple carry adder of the last example:



- Note: The "long path" is from  $A_0$  or  $B_0$  through the circuit to  $S_3$ .


## Carry Lookahead Adders

- optimize design by looking at equations for the  $C_i$  (carry ins) in terms of all the bit inputs



so  $C(i+1) = \text{function}(X_0, \dots, X_i, Y_0, \dots, Y_i, C_0)$

rather than  $C(i+1) = X_i Y_i + C_i (X_i + Y_i)$

IDEA

 


# Carry Look Ahead

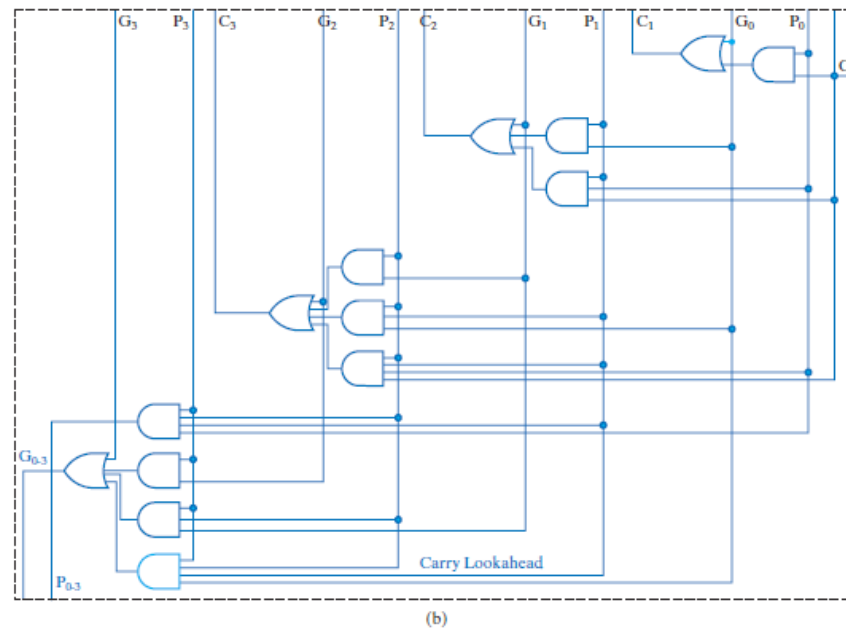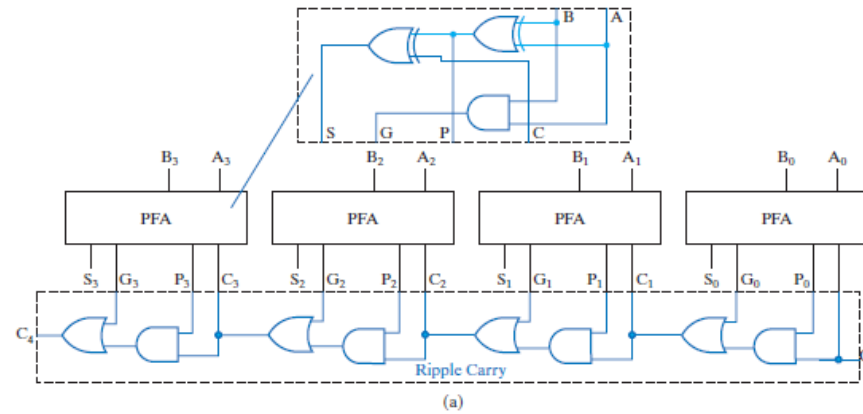


 
# 2's Complement Adder/Subtractor

- Subtraction can be done by addition of the 2's Complement.
  - Complement each bit (1's Complement.)
  - Add 1 to the result.
- The circuit shown computes  $A + B$  and  $A - B$ :
- For  $S = 1$ , subtract, the 2's complement of  $B$  is formed by using XORs to form the 1's comp and adding the 1 applied to  $C_0$ .
- For  $S = 0$ , add,  $B$  is passed through unchanged



# Arithmetic Logic Unit

447-453

**Sample ALU:**  
word F

input words A, B and output

control lines M, S1, S0 and carry-in C0

## M = 0, Logical Bitwise Operations

S1	S0	Function	Comment
0	0	$F_i = A_i$	Input $A_i$ transferred to output
0	1	$F_i = \text{not } A_i$	Complement of $A_i$ transferred to outp
1	0	$F_i = A_i \text{ xor } B_i$	Compute XOR of $A_i, B_i$
1	1	$F_i = A_i \text{ xnor } B_i$	Compute XNOR of $A_i, B_i$

## M = 1, C0 = 0, Arithmetic Operations

0	0	$F = A$	Input A passed to output
0	1	$F = \text{not } A$	Complement of A passed to output
1	0	$F = A \text{ plus } B$	Sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B$	Sum of B and complement of A

## M = 1, C0 = 1, Arithmetic Operations

0	0	$F = A \text{ plus } 1$	Increment A
0	1	$F = (\text{not } A) \text{ plus } 1$	Twos complement of A
1	0	$F = A \text{ plus } B \text{ plus } 1$	Increment sum of A and B
1	1	$F = (\text{not } A) \text{ plus } B \text{ plus } 1$	B minus A