


12 Introduction to Sequential Circuits

©Department of Computer Science
University of Victoria

SEQUENTIAL CIRCUITS

We now add memory!

 - output depends on both current AND past inputs
- feedback



- ❖ the binary information stored in memory elements defines the **STATE** of the sequential circuit
- ❖ **TIMING**: if things are not in perfect sequence, we might be looking at the incorrect output
- ❖ **NEXT STATE**: depends on current state plus current inputs

Synchronous and Asynchronous

❖ synchronous

- changes in output occur at discrete instants of time
- there is a clock which synchronizes all circuit elements


❖ asynchronous

- behaviour depends on order of input changes
- does not wait for clock pulses
- wanting speed, cannot afford to wait for clock signal, control signals from interrupts, etc.

Memory Elements


Flip-Flops, Latches,

→ single bit storage devices

 

S	R	Q
0	0	unchanged
0	1	goes to 0
1	0	goes to 1


SET / RESET (R - S) Latch

 


		nor
0	0	1
0	1	0
1	0	0
1	1	0

S	R	P	Q	
0	0	1	0	stable: Q = 0
1	0	0	1	set
0	0	0	1	stable: Q = 1
0	1	1	0	reset
0	0	1	0	stable: Q = 0


s 0 → 1 → 0

 

s 0

 

Another View

 

IF $S = R = 0$, then

0 to a NOR input makes it an inverter

\Rightarrow we have 2 inverters in a closed loop

\Rightarrow whatever is in the system, stays there,


\Rightarrow keeps circulating

\Rightarrow we have memory

Details

restrict the inputs so that $R=S=1$ is not allowed (unstable),

 → then P , Q are always complements of each other



$S=1, R=0$, → Q' to 0, → Q to 1, → FF is set


back to $S = R = 0$, keeps $Q' = 0$ and $Q = 1$

change R to 1 ($S=0$), → Q to 0, → Q' to 1, → FF is reset

back to $S = R = 0$, keeps $Q = 0$ and $Q' = 1$

State Table

present state			next state		
S(t)	R(t)	Q(t)	Q(t + 1) or Q+		
0	0	0	0	} stable	
0	0	1	1		
0	1	0	0	} reset	
0	1	1	0		
1	0	0	1	} set	
1	0	1	1		
1	1	0	X	###	NOT
1	1	1	X	###	USED

 

Characteristic Equation

S(t)	R(t)	Q(t)	Q+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	X
1	1	1	X

map for $Q (t + 1)$ or $Q+$

		R(t) Q(t)			
		00	01	11	10
S(t)	0		1		
	1	1	1	X	X

$$Q (t + 1) = S (t) + R' (t) Q (t)$$

Characteristic Equation is:

$$Q^+ = S + R' Q \quad S R = 0$$

What does the characteristic equation mean?

Characteristic Equation

$$Q^+ = Q(t+1) = S + R'Q \quad SR = 0$$

it means :

(1) ***next state = 1*** IF

(a) it is set to 1 by putting S to 1

or


(b) present state =1 and it is not reset


(2) SR=0 means S=R=1 is not allowed

CLOCKED R - S Latch

Level-Sensitive R - S Latch

 - a **clock** or **enable** is necessary to maintain the circuit allowing changes at predetermined discrete moments






 


- ❖ outputs r1 and s1 are 0 as long as enable is 0
→ SR latch stable
- ❖ when enable goes to 1, the S and R inputs are allowed through to set/reset the basic latch
- ❖ S,R inputs can change while enable is 0, but latch is only activated when enable becomes 1

NAND implementation for SR

nand	0	1
0	1	1
1	1	0

  

  

opposite of NOR: LOW CONTROL


$\overline{S}\overline{R}$ Latch

SR TABLE (Nand)

present state <div> $S(t)$ $R(t)$ $Q(t)$ </div>			next state <div> $Q(t+1)$ </div>	
0	0	0	X	} not allowed
0	0	1	X	
0	1	0	1	} set
0	1	1	1	
1	0	0	0	} reset
1	0	1	0	
1	1	0	0	} stable
1	1	1	1	

Look carefully at
CLOCKED NAND FF
and the
characteristic
equation


Common circuit, as used in the lab

 

follows primary SR table

C	S	R	Q ⁺
0	x	x	No change
1	0	0	No Change
1	0	1	Q=0
1	1	0	Q=1
1	1	1	Undefined


TOGGLE (T) Flip Flop

 

$T=0$, no change

$T=1$, flip state

$T : 0 \rightarrow 1$

 


T	Q	Q ⁺
0	0	0
0	1	1
1	0	1
1	1	0

$$Q^+ = T' Q + T Q'$$

$$= T \oplus Q$$

D Flip Flop

 

D for DATA

→ transferring data into a FF
(typical memory element)



D	Q	Q ⁺
0	0	0
0	1	0
1	0	1
1	1	1

state Q^+ of FF after clock
pulse is equal to the input
D before the clock pulse

$$Q^+ = D$$


next state equation

  Removes the
undefined state
of $S=R=1$ by using
inverter!!



$$Q^+ = D$$


STABLE STATE

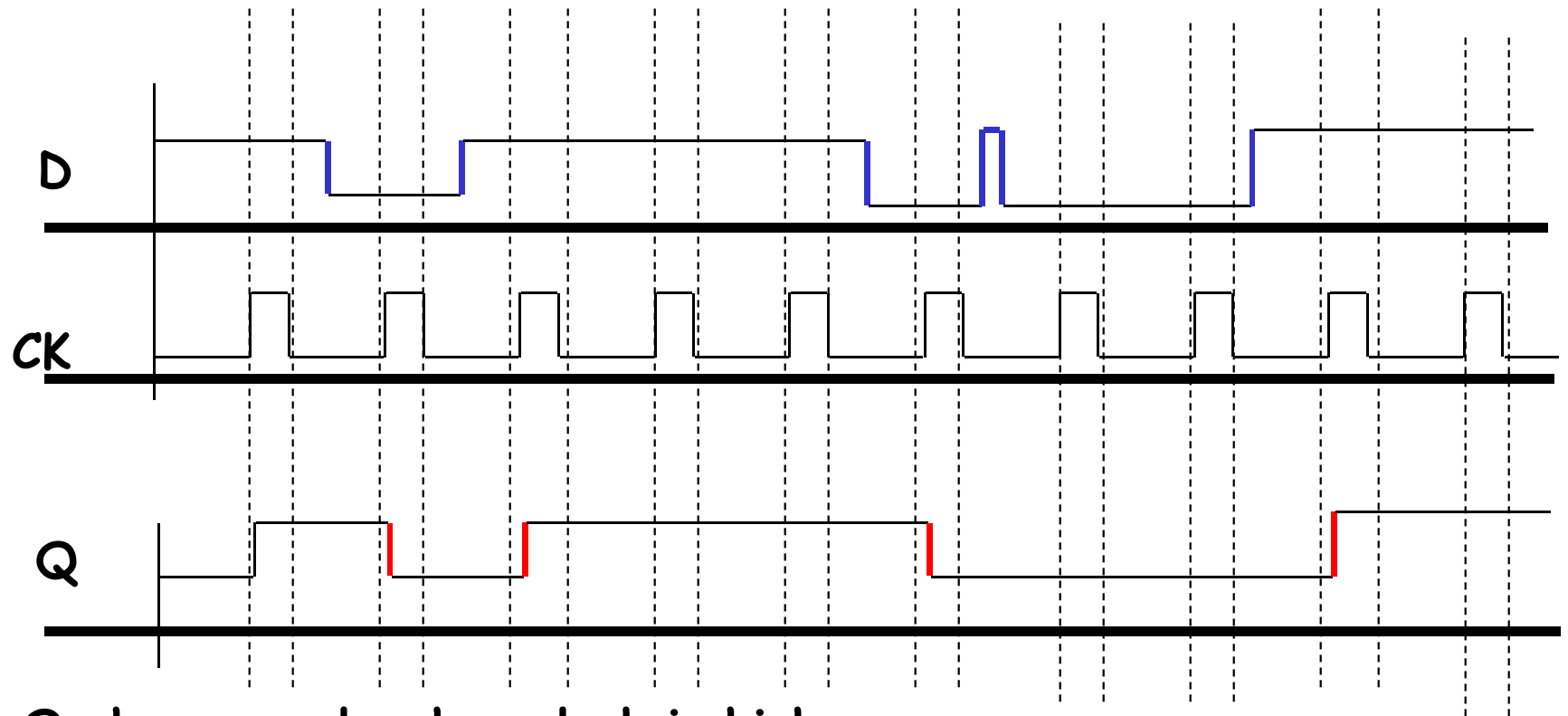

- Q changes only when clock is high
- here it shows that it changes after the clock has been high
- D gets changed when clock is low and can be changed many times without any effect (while clock is low)

J K Flip Flops

 → they combine SR and T, eliminating invalid inputs



❖ when both J and K are 0, stable, no change

❖ when both J and K are 1, it acts as T (toggles)

❖ when either J or K are 1, but not both, it acts as SR

STATE TABLE FOR J K

present state

next state

J	K	Q(t)	Q(t+1)	
0	0	0	0	stable
0	0	1	1	
0	1	0	0	reset
0	1	1	0	
1	0	0	1	set
1	0	1	1	
1	1	0	1	toggle
1	1	1	0	


Next State Equation - Characteristic Equation

		J	
		0	1
KQ	00		1
	01	1	1
	11		
	10		1


Q^+

$$Q^+ = \overline{K} Q + J \overline{Q}$$

JK Flip Flop from SR FF (example)

 

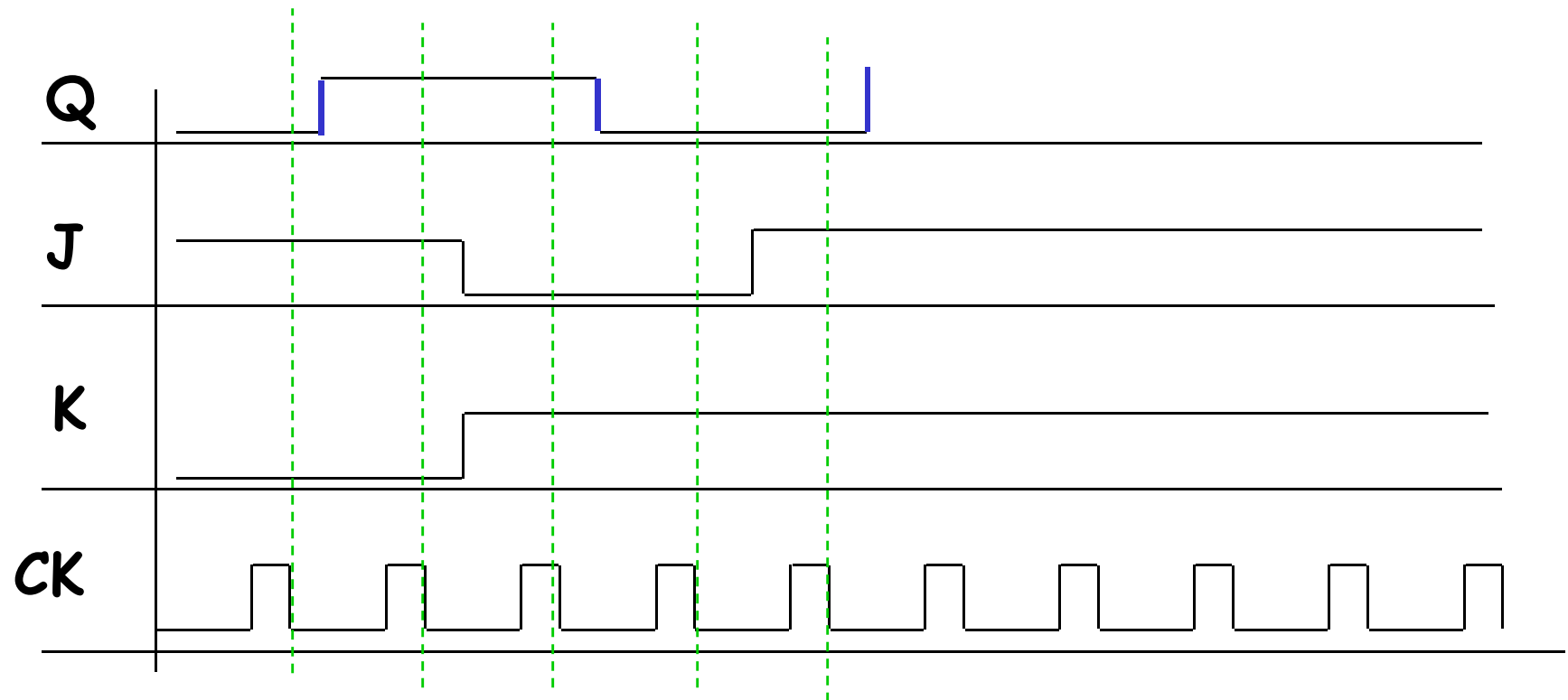- ❖ when $CK = 0$, nothing happens
- ❖ when $CK=1$ and $Q = 0$, then $R = 0$
and $S = J \rightarrow$ it will set or stay stable
- ❖ when $CK=1$ and $Q = 1$, then $S = 0$
and $R = K \rightarrow$ it will reset or stay stable
- ❖ when $J = K = 1$, it toggles (flips state)



- state Q changes short time after trailing edge of clock
- change in state always initiated by clock pulse, not by changes in J or K
- if clock remains 1 while $J=K=1$, it keeps flipping
- clock must have time duration shorter than gates propagation when used in feedback loops (difficult)

(use master-slave or edge triggered FF - later)

Characteristic Equations


$$\text{S-R : } Q^+ = \bar{R} Q + S \quad (SR = 0)$$

$$\text{T : } Q^+ = \bar{T} Q + T \bar{Q}$$


$$\text{J-K : } Q^+ = \bar{K} Q + J \bar{Q}$$

$$\text{D : } Q^+ = D$$

Master-Slave J-K FF


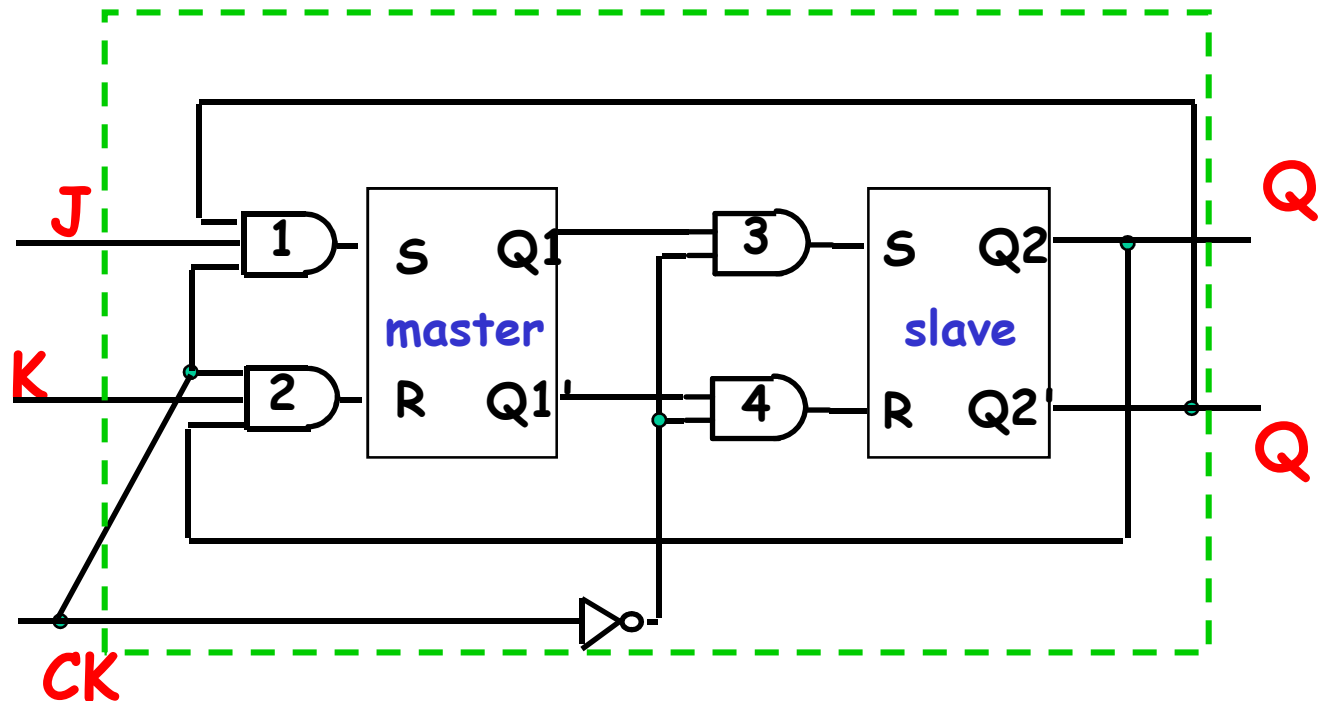


 - when $CK=1$, only gates 1 & 2 operate, setting or resetting master FF (Q_1)
- when $CK=0$, only gates 3 & 4 operate, setting or resetting slave FF (Q_2)
- one FF is always isolated and maintains state




  Q1 changes at *leading edge* ,Q2 changes *trailing edge*

- master operates at *leading edge* of clock
- slave operates at *trailing edge* of clock
- any changes in J,K primary inputs must occur when the master is isolated (clock=0)
- outputs are read after trailing edge



Direct Inputs

 

J K flip flop with
preset and clear

At power up or at reset, all or part of a sequential circuit usually is initialized to a known state before it begins operation

This initialization is often done outside of the clocked behavior of the circuit, i.e., asynchronously

Latch Problems

- ❖ The change in the flip-flop output is delayed by the pulse width which makes the circuit slower
- ❖ S and/or R may change while $C = 1$
 - This behavior is called *1s catching*


Flip-Flop Solution

- ❖ Use edge-triggering instead of latches or master-slave
- ❖ An *edge-triggered* flip-flop ignores the pulse while it is at a constant level and triggers only during a *transition* of the clock signal

Edge-Triggered D Flip-Flop


The edge-triggered D flip-flop is similar to a master-slave D flip-flop

 - It can be formed by:
 - Replacing the first clocked S-R latch with a clocked D latch or
 - Adding a D input and inverter to a master-slave S-R flip-flop




The change of the D flip-flop output is associated with the *negative edge* at the end of the pulse → called a *negative-edge triggered flip-flop*

Positive-Edge Triggered D Flip-Flop

 


Formed by adding inverter to clock input


Negative Edge-Triggered D Flip Flop

 


Negative Edge-Triggered D Flip Flop

 


Negative Edge-Triggered D Flip Flop

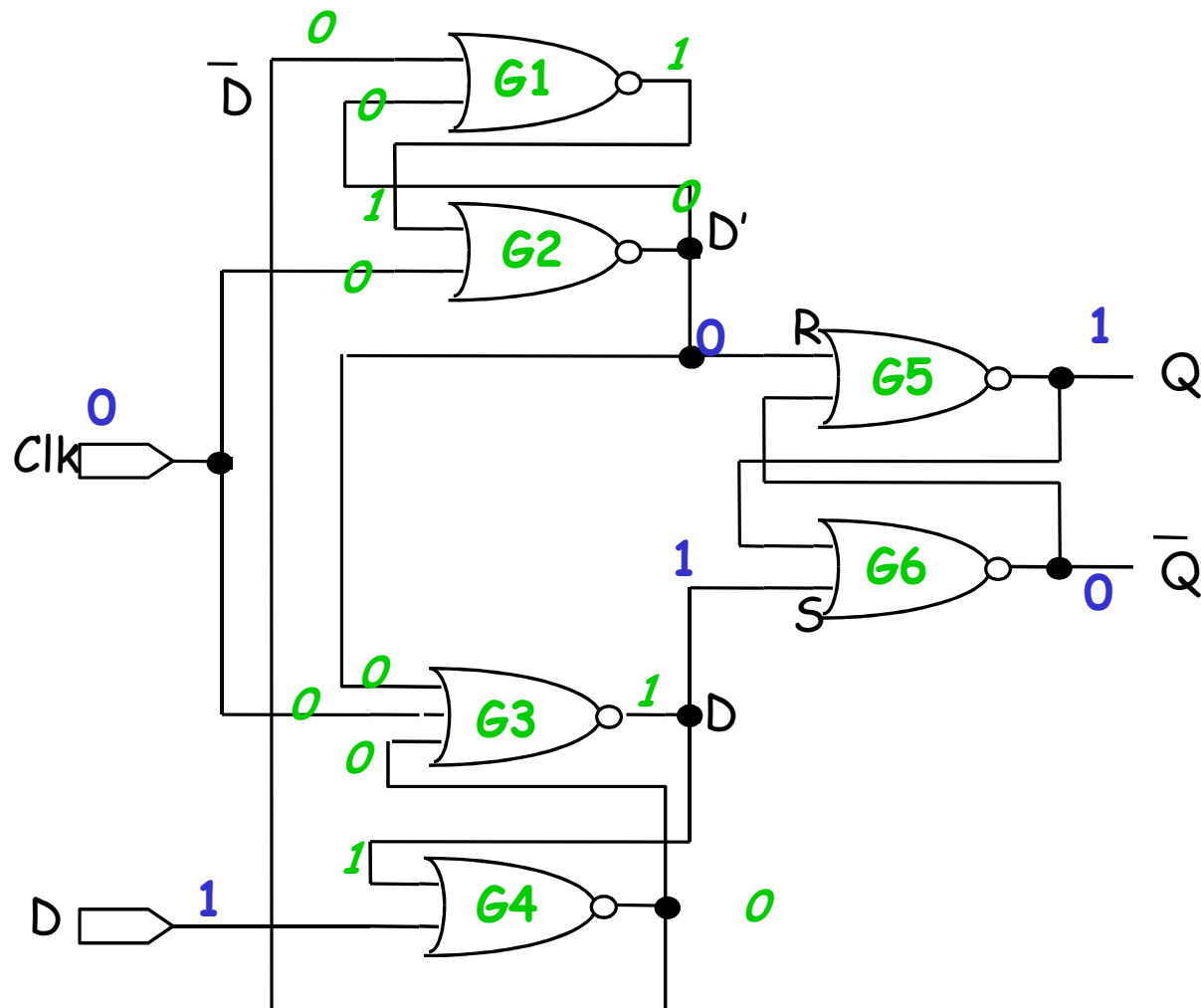

Negative Edge-Triggered D Flip Flop

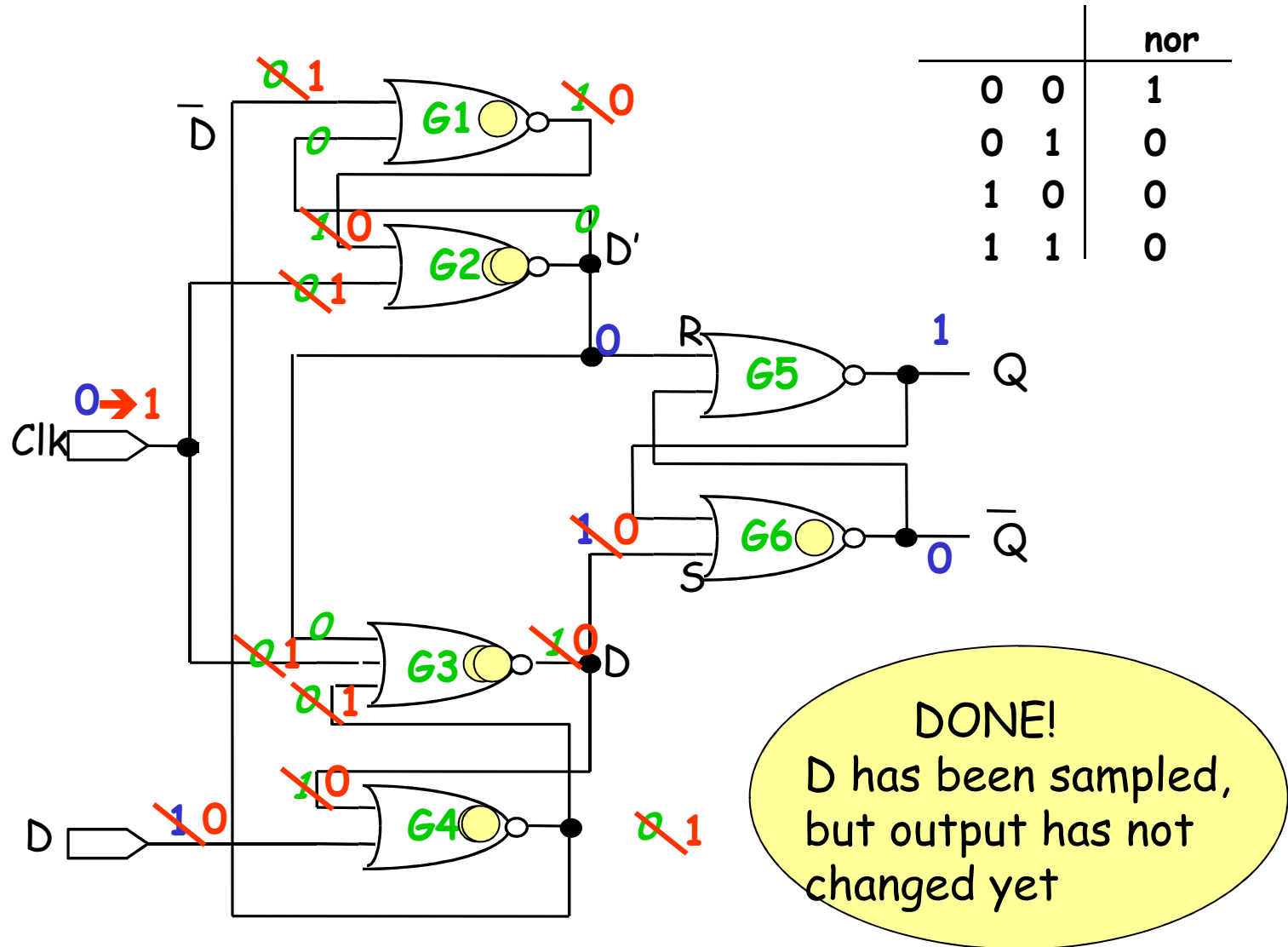


Negative Edge-Triggered D Flip Flop

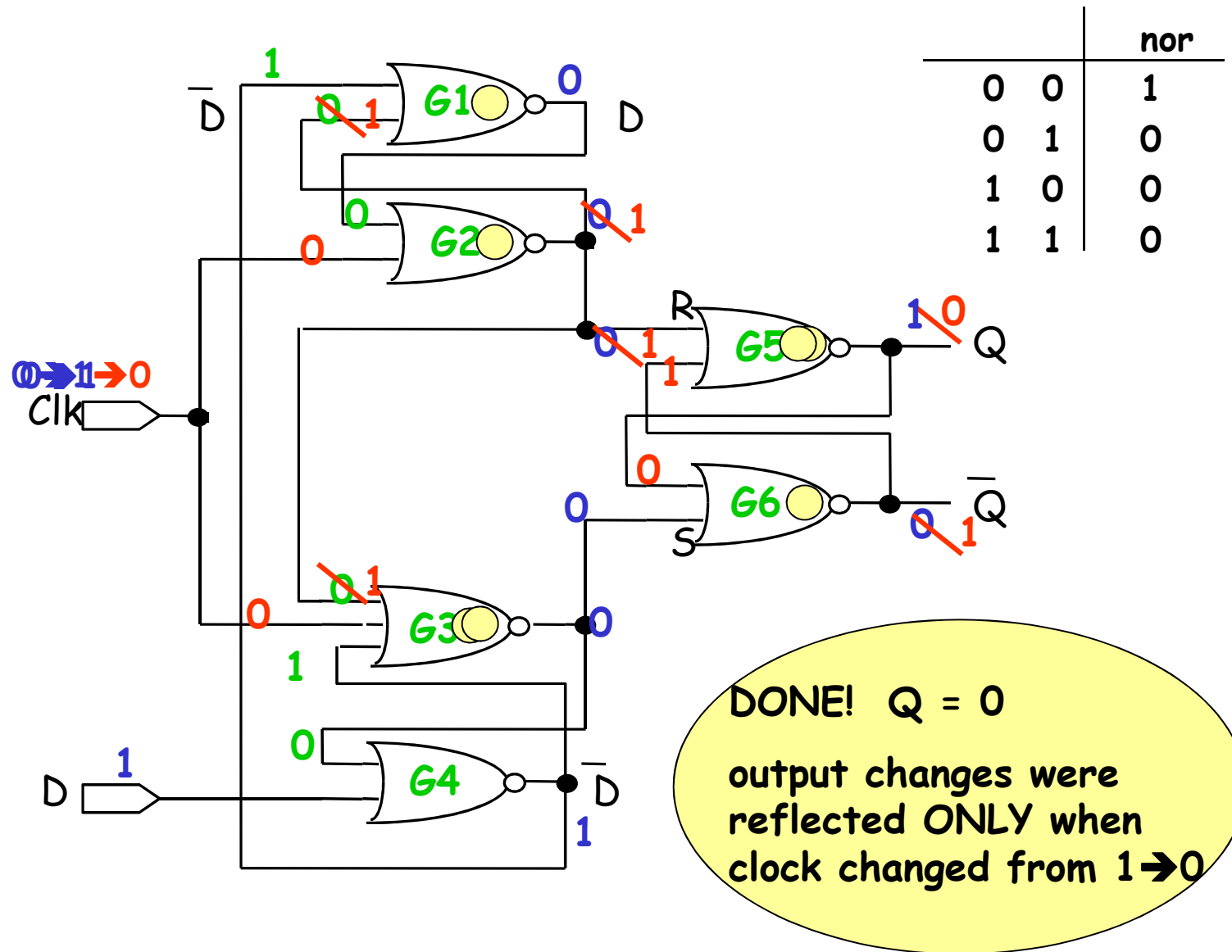

Latches versus Flip-Flops


Type	Inputs Sampled	Outputs Valid
Unclocked latch	always	prop. delay from input change
Level sensitive	clock high	prop. delay from input change
Positive edge flip-flop	Clock Lo-to-Hi	prop. delay from rising edge
Negative edge flip-flop	Clock Hi-to-Lo	prop. delay from trailing edge
Master/slave flip-flop	Clock Hi-to-Lo	prop. delay from trailing edge

Standard Symbols for Storage Elements

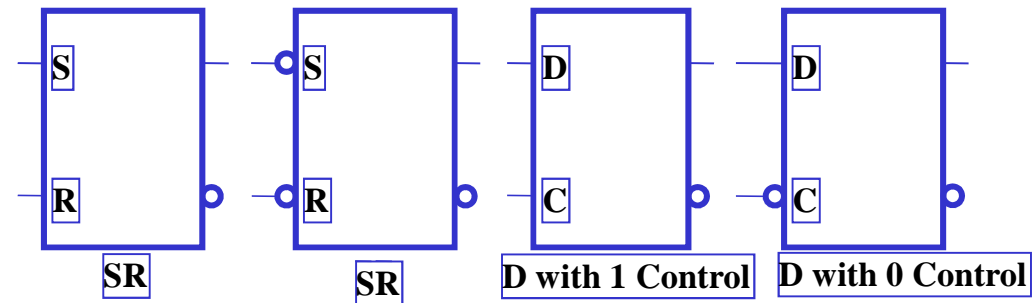

 
(a) Latches

- Master-Slave:
Postponed output
indicators



(b) Master-Slave Flip-Flops

- Edge-Triggered:
Dynamic
indicator

 

(c) Edge-Triggered Flip-Flops